
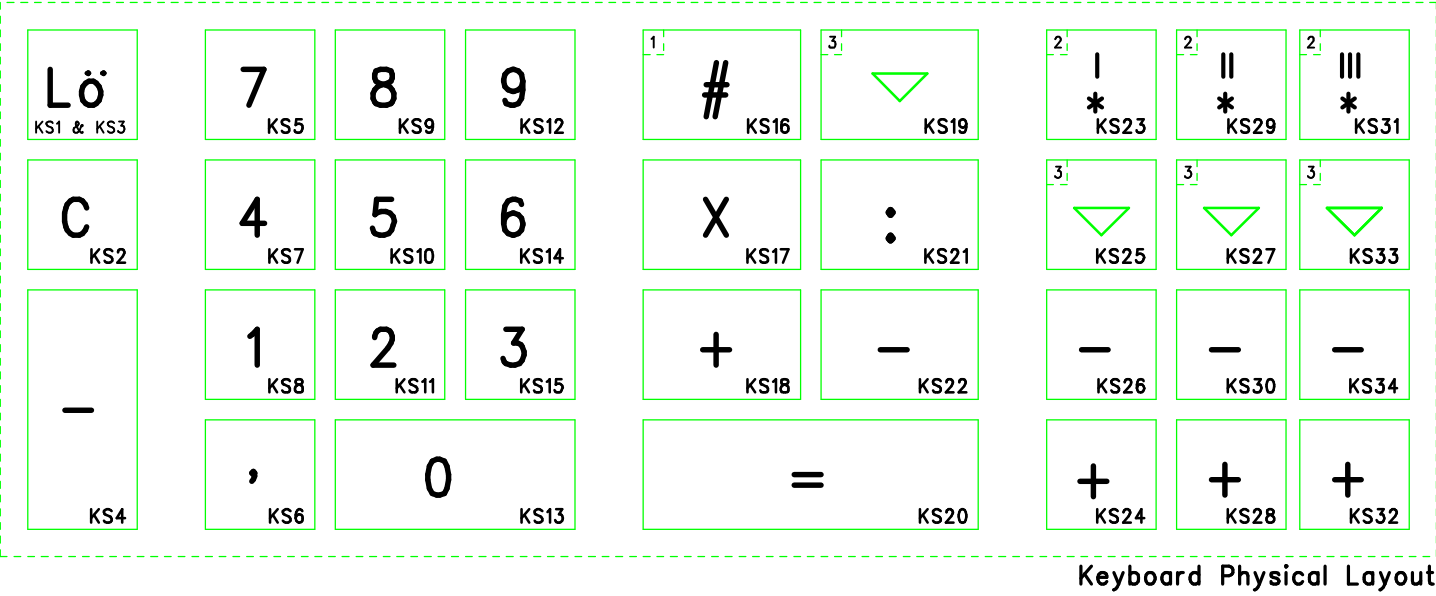


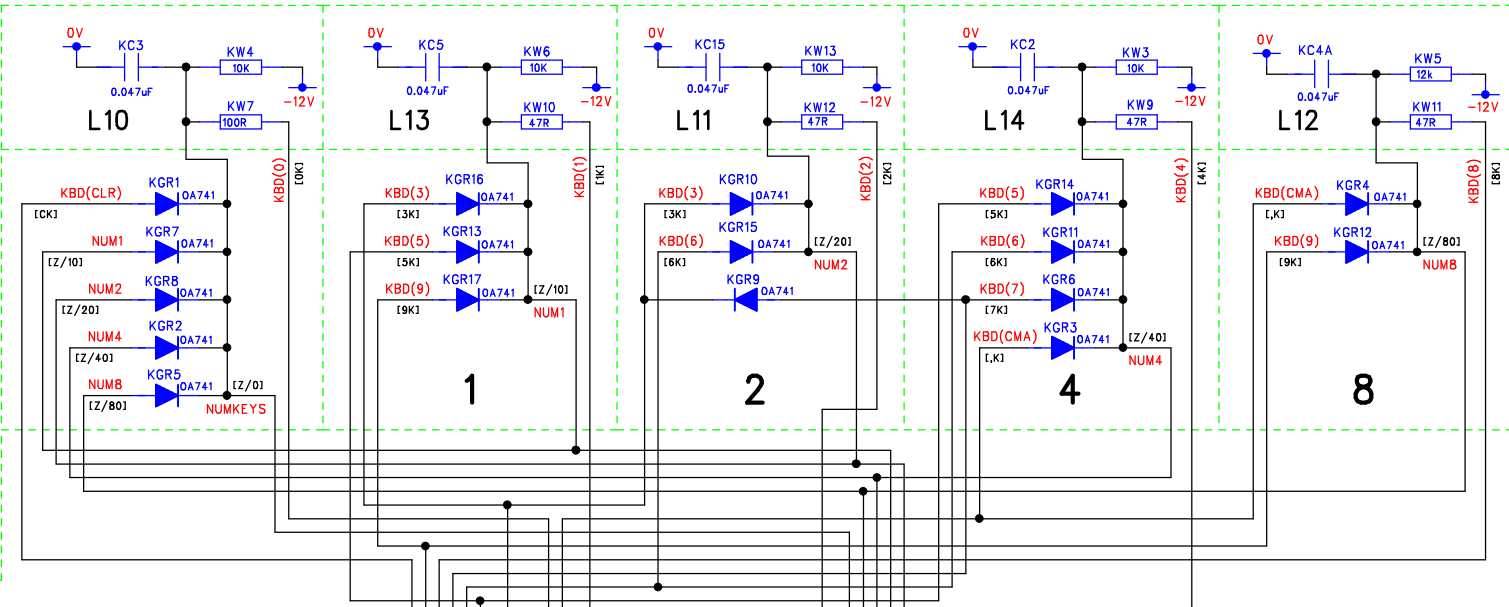


Notes -

1	#	Exchange operands	4	-	Negate entry
2	I II III	Recall (clears memory)			
3	✓	Recall only			

RevNo	Revision note	Date	By	Checked
-	-	-	-	-



Keyboard PCB 224-301-014a

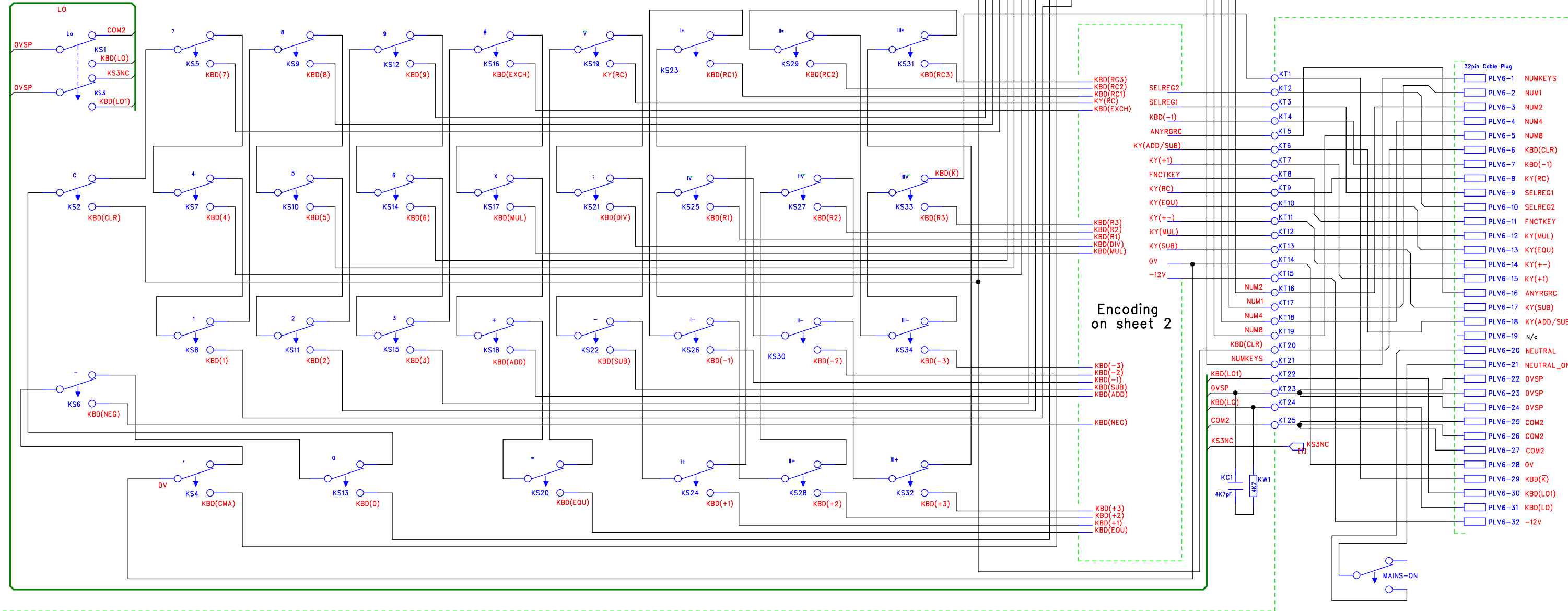

Encoding on sheet 2

Keyboard & Digit Key Encoder

These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V



DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

Pcb Dwg # =


Name	Date
MD Hatch	15/8/2017
Checked	-

Scale Nts

Sheet	1
Next Sheet	2
Drawing Number	Soemtron 222

Title
Soemtron ETR 222 Calculator
[Keyboard Circuit & Layout]
[PCB = 224-301-014a]

A2 Issue A

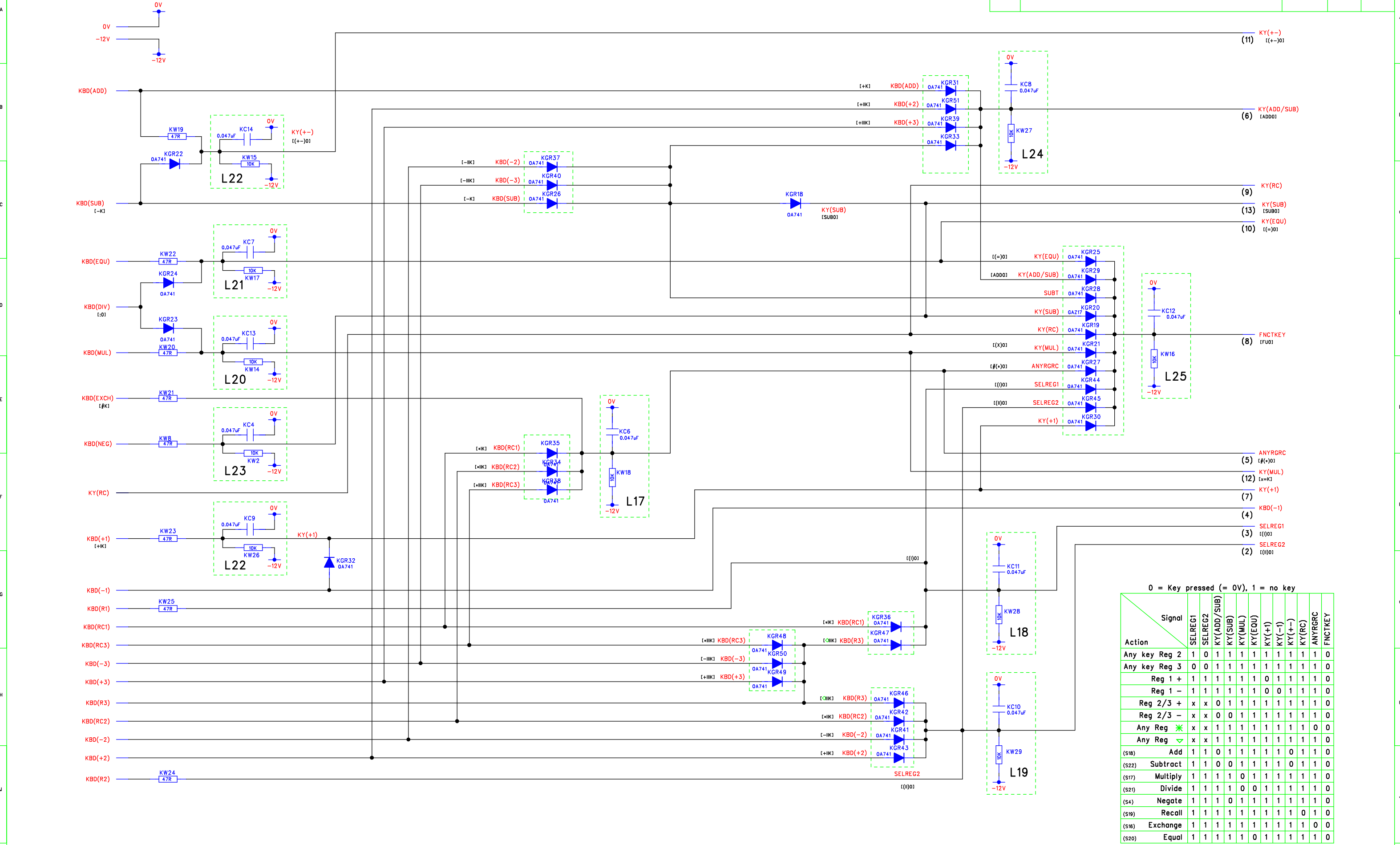

0 = Key pressed (= 0V), 1 = no key												
Signal	SELREG1	SELREG2	KY(ADD/SUB)	KY(SUB)	KY(MUL)	KY(EQU)	KY(+)	KY(-)	KY(+/-)	ANYRCRC	FNCTKEY	
Action												
Any key Reg 2	1	0	1	1	1	1	1	1	1	1	0	
Any key Reg 3	0	0	1	1	1	1	1	1	1	1	0	
Reg 1 +	1	1	1	1	1	1	0	1	1	1	0	
Reg 1 -	1	1	1	1	1	1	0	0	1	1	0	
Reg 2/3 +	x	x	0	1	1	1	1	1	1	1	0	
Reg 2/3 -	x	x	0	0	1	1	1	1	1	1	0	
Any Reg *	x	x	1	1	1	1	1	1	1	1	0	
Any Reg <	x	x	1	1	1	1	1	1	1	1	0	
(S18) Add	1	1	0	1	1	1	1	1	0	1	0	
(S22) Subtract	1	1	0	0	1	1	1	1	0	1	0	
(S17) Multiply	1	1	1	1	0	1	1	1	1	1	0	
(S21) Divide	1	1	1	1	0	0	1	1	1	1	0	
(S4) Negate	1	1	1	0	1	1	1	1	1	1	0	
(S19) Recall	1	1	1	1	1	1	1	1	0	1	0	
(S16) Exchange	1	1	1	1	1	1	1	1	1	0	0	
(S20) Equal	1	1	1	1	1	0	1	1	1	1	0	

Function & Register Key Encoder

These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V



© 2017 Mike Hatch. (www.soemtron.org)

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

Pcb Dwg # =

	Name	Date
Drawn	MD Hatch	28/02/2024
Checked	-	-

Scale

Nts

Sheet

2

Next Sheet

3

Drawing Number

Title
Soemtron ETR 222 Calculator
Keyboard Function Encoding
Circuit Diagram



Soemtron 222

A2 Issue

A

PCB = 05-222-0000-5b (comp)
PCB = 05-222-0000-5a (track)


RevNo	Revision note	Date	By	Checked
-	-	-	-	-

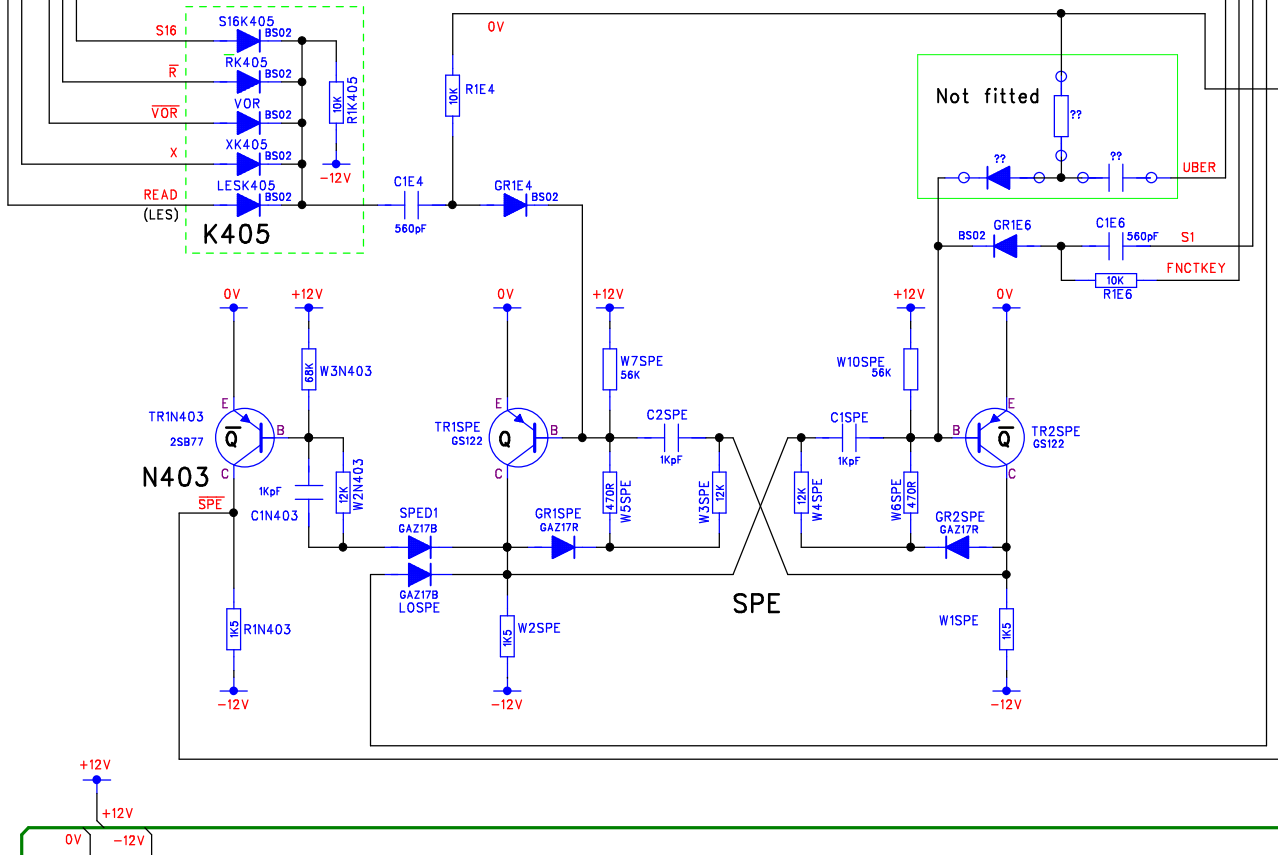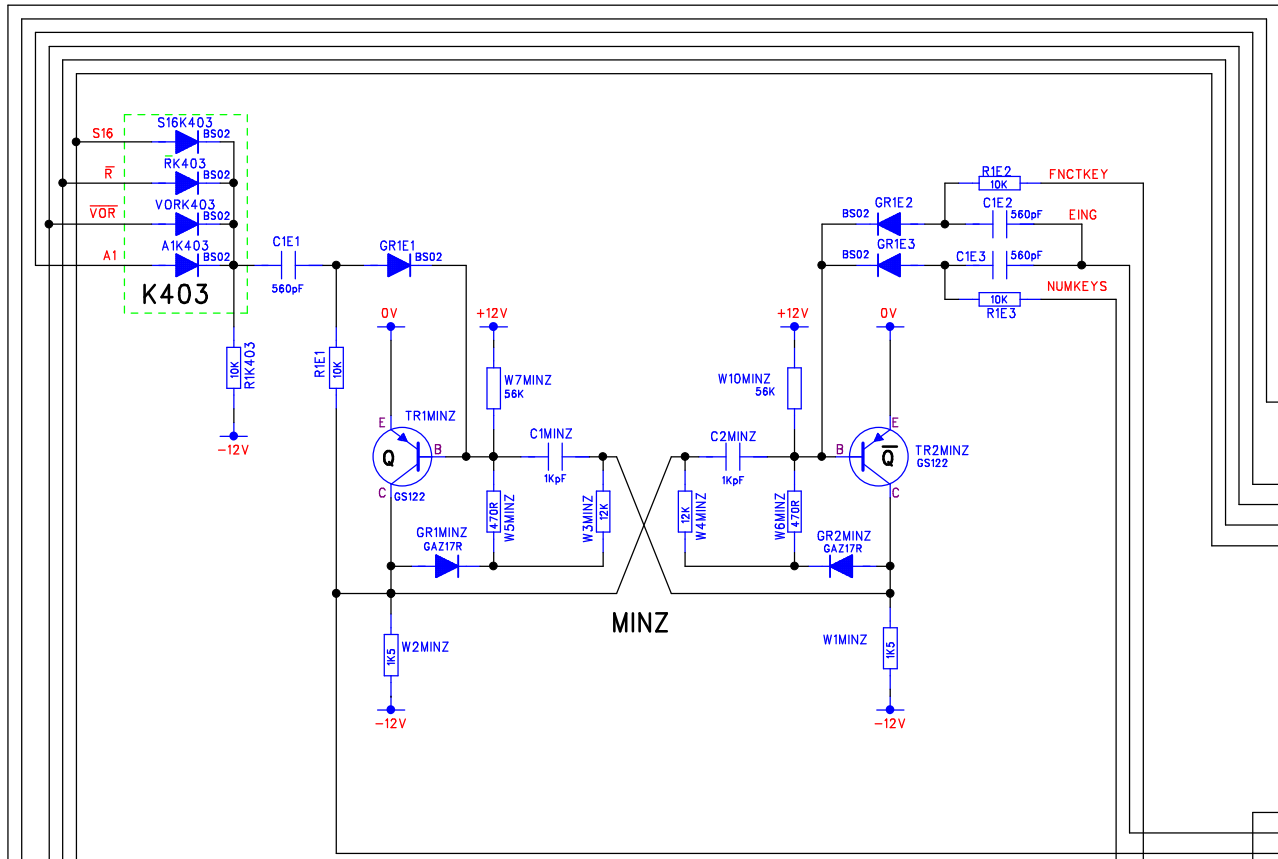

These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V

- UKBD [4,5,6]
- RU -10V
- CATHODE9
- CATHODE8
- CATHODE7
- X
- AB
- CATHODE6
- CATHODE5
- CATHODE4
- CATHODE3
- CATHODE2
- CATHODE1
- CATHODE0
- VER
- A2
- A4
- AT
- A4
- X
- N401
- A2
- A1
- VOR
- R
- S16
- E
- F6
- DIV
- K404
- READ
- U
- KBD(R)
- CB
- C2
- C1
- Z
- C4
- S1
- EING
- MINZ
- UBER
- FNCTKEY
- NUMKEYS
- KBD(L01)
- SPE
- N405
- N401
- STF
- KEYPRES
- 0V
- +12V
- 12V
- 12V
- ANODE15
- DRV14
- ANODE14
- DRV15
- DRV11
- DRV10
- DRV9
- DRV12
- DRV13
- ANODE13
- ANODE12
- ANODE11
- ANODE10
- ANODE9
- DRV7
- DRV8
- DRV6
- DRV5
- DRV4
- DRV3
- DRV2
- DRV1
- ANODE8
- ANODE7
- ANODE6
- ANODE5
- ANODE4
- ANODE3
- ANODE2
- ANODE1
- +190V(1)
- +90V


- 1 = LHS (Track side)
- UK1 Yellow
- UK2 Black
- UK3 Yellow
- UK4 White
- UK5 Black
- UK6 White
- UK7 Black
- UK8 Yellow
- UK9 White
- UK10 Black
- UK11 Yellow
- UK12 White
- UK13 Black
- UK14 Black
- UK15 Black
- UK16 Yellow
- UK17 White
- UK18 Black
- UK19 Black
- UK20 Black
- UK21 Black
- UK22 N/c
- UK23 Black
- UK24 Black
- UK25 White
- UK26 Black
- UK27 Yellow
- UK28 White
- UK29 White
- UK30 White
- UK31 White
- UK32 White
- UK33 White
- UK34 Yellow
- UK35 Yellow
- UK36 Black
- UK37 Yellow
- UK38 Black
- UK39 White
- UK40 Yellow
- UK41 White
- UK42 White
- UK43 Yellow
- UK44 White
- UK45 Black
- UK46 Yellow
- UK46A Yellow
- UK47 Yellow
- UK48 White
- UK49 White
- UK50 Black
- UK51 Yellow
- UK52 White
- UK53 White
- UK54 White
- UK55 White
- UK56 Black
- UK57 Yellow
- UK58 White
- UK59 Black
- UK60 Black
- UK61 Yellow
- UK62 Yellow
- UK63 Black
- UK64 Yellow
- UK65 White
- UK66 Black
- UK67 Yellow
- UK68 White
- UK69 Black
- UK70 White
- UK71 Yellow
- UK72 White
- UK73 Black
- UK74 Yellow
- UK75 White
- UK76 Black
- UK77 Black
- UK78 Yellow
- UK79 White
- UK80 Black
- UK81 Yellow
- UK82 White
- UK83 Black
- UK84 Yellow
- UK85 White
- UK86 White
- 86 = RHS (Track side)

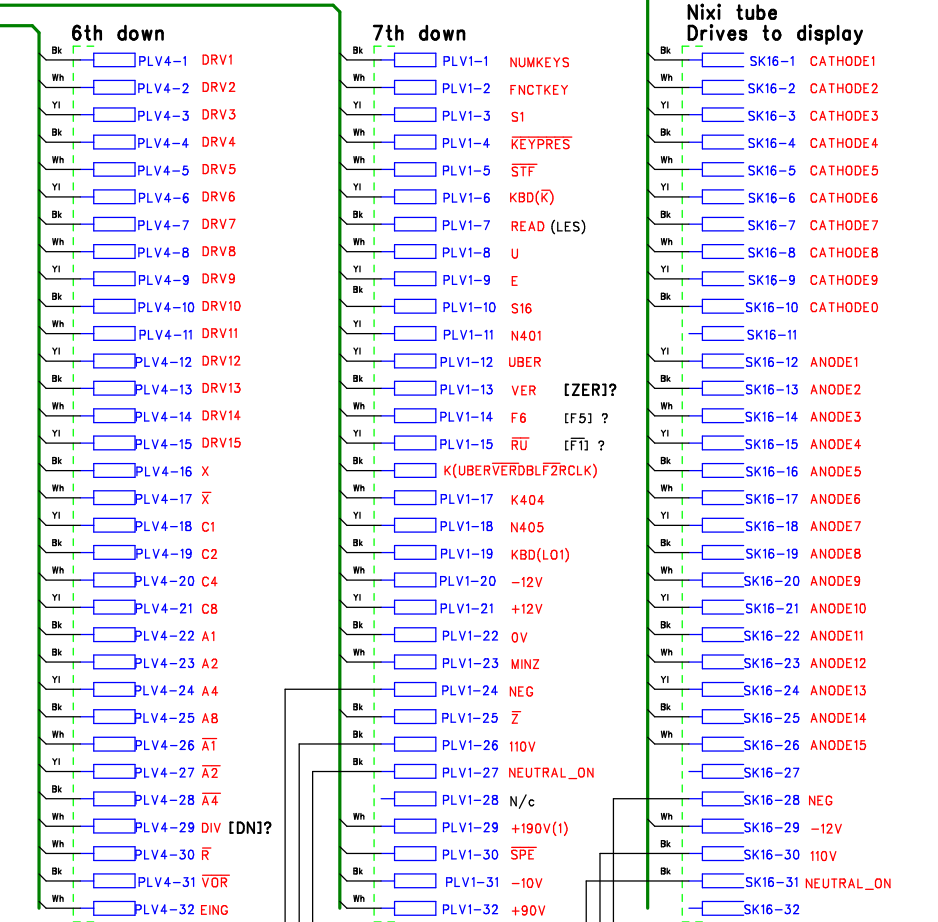

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org




Pcb Dwg # =			Scale	Nts	Title	
			Sheet	3	Soemtron ETR 222 Calculator	
Drawn			Next Sheet	4	Display Drivers Under Keyboard PCB	
Checked			Drawing Number		Soemtron 222	
					A2	Issue A

RevNo	Revision note	Date	By	Checked
—	—	—	—	—

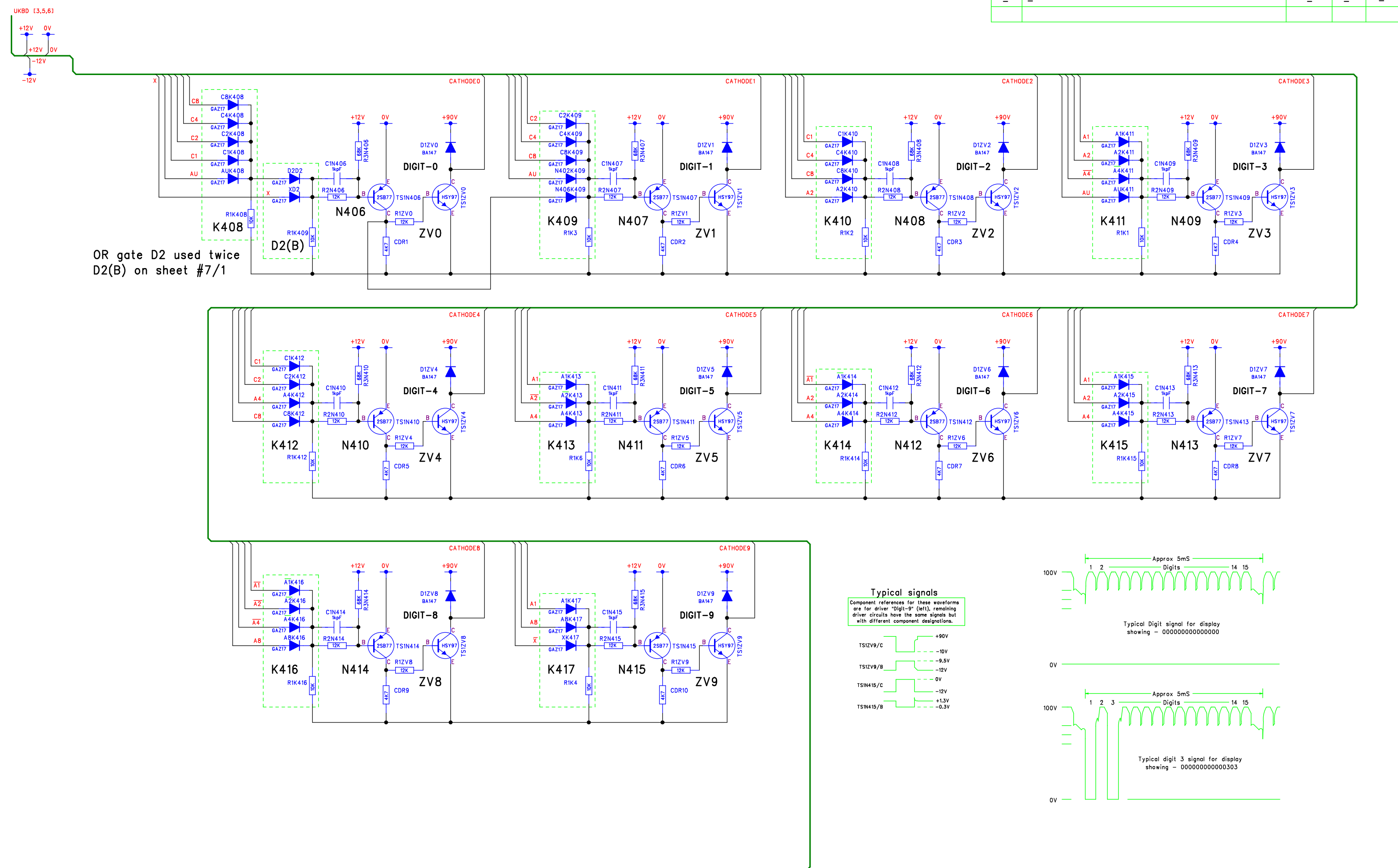

OR gate D2 used twice
D2(B) on sheet #7/1

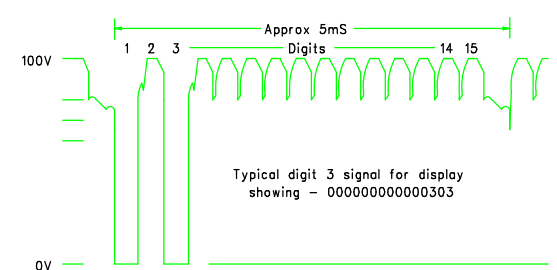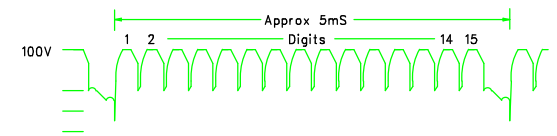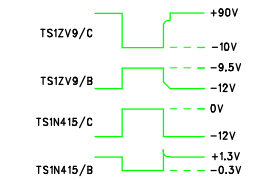Typical signals
Component references for these waveforms are for driver "Digit-9" (left), remaining driver circuits have the same signals but with different component designations.



- Notes:
1. All wire 24 AWG minimum unless specified otherwise
 2. All mains wire to be 18 AWG, 600V




© 2018 Mike Hatch. (www.soemtron.org)

McLENNAN SERVO SUPPLIES LTD.
Unit 1, The Royston Centre
Lynchford Road, Ash Vale UK GU12 5PQ
Tel : 01252 531444 / Fax: 01252 531446
www.mclennan.co.uk

Pcb Dwg # =		
Drawn	Name	Date
Checked	MD Hatch	20/11/2018



DO NOT MANUFACTURE FROM NUMERICAL ISSUE DRAWINGS			
Scale	Nts	Title	
Sheet	4	Soemtron ETR 222 Calculator	
Next Sheet	5	Transcribed Misc Circuits	
Drawing Number	XXXX	Display Drivers PCB – Cathode Drivers	
A2		Issue	A

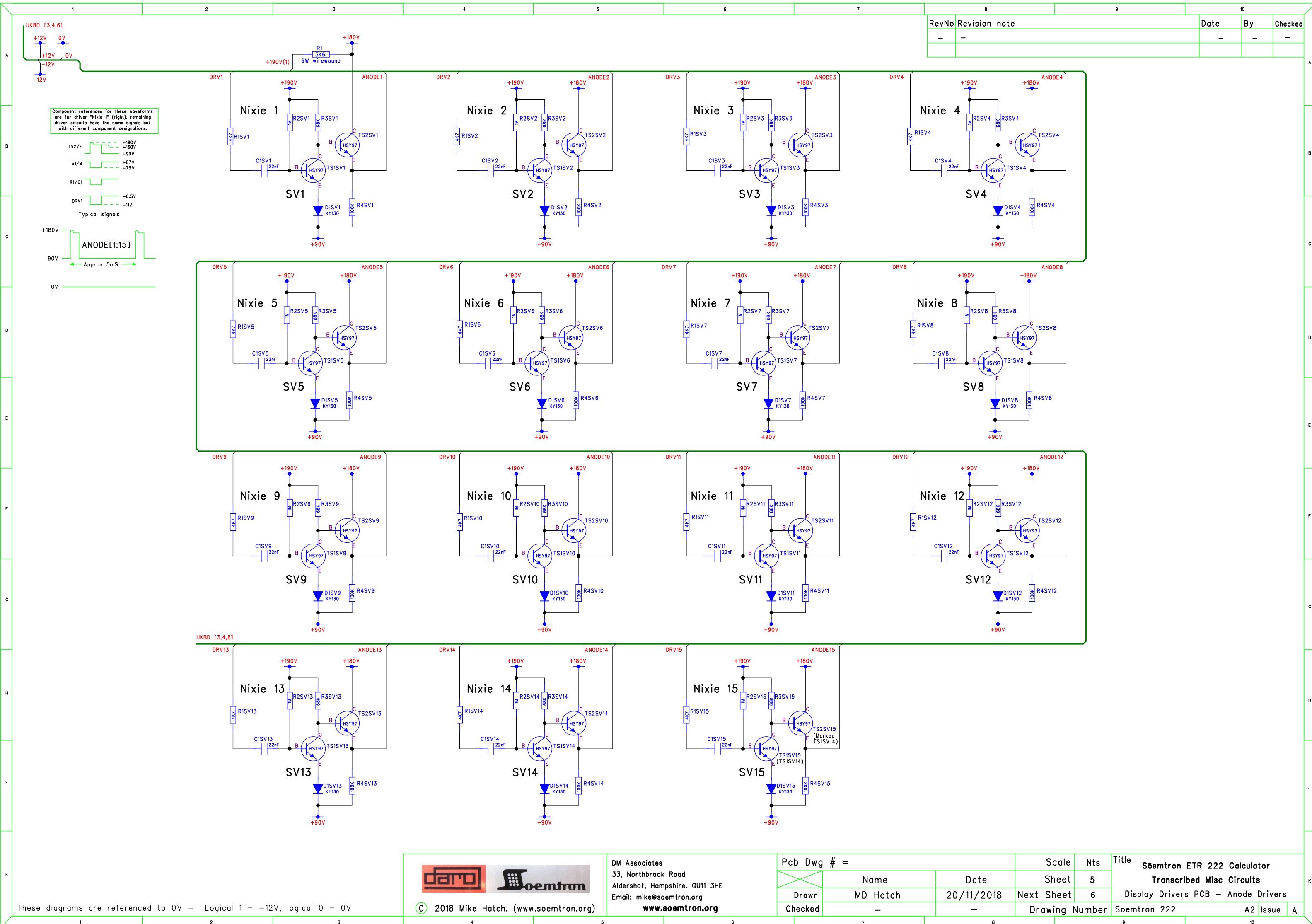

RevNo	Revision note	Date	By	Checked
-	-	-	-	-

Decimal Point Switch Wiring Table (X=0V)

Switch position →		1	2	3	4	5	6	7	8	9	10	11	12
Pin	Function	0	1	2	3	4	6	Z	9	10	11	12	14
KS1D	PL4/1	2	X										
"	PL4/2	3		X									
"	PL4/3	4			X								
"	PL4/4	5				X							
"	PL4/5	6					X						
"	PL4/6	8						X					
"	PL4/7	9							X				
"	PL4/8	10								X			
"	PL4/9	11									X		
"	PL4/10	12										X	
KS1B	PL3/1	G11	X		X		X	X		X	X	X	X
"	PL3/2	G14				X	X	X			X	X	X
KS1C	PL3/3	G18							X	X	X	X	X
KS1B	PL3/4	G21		X		X			X		X		
KS1A	PL3/5	G22		X	X		X		X	X			X
"	PL3/6	G24		X	X	X	X		X	X	X	X	
KS1D	PL3/7	G28		X	X	X	X	X		X	X	X	X
KS1A/B	PL3/9	DIV01K		X	X	X	X	X		X	X	X	X

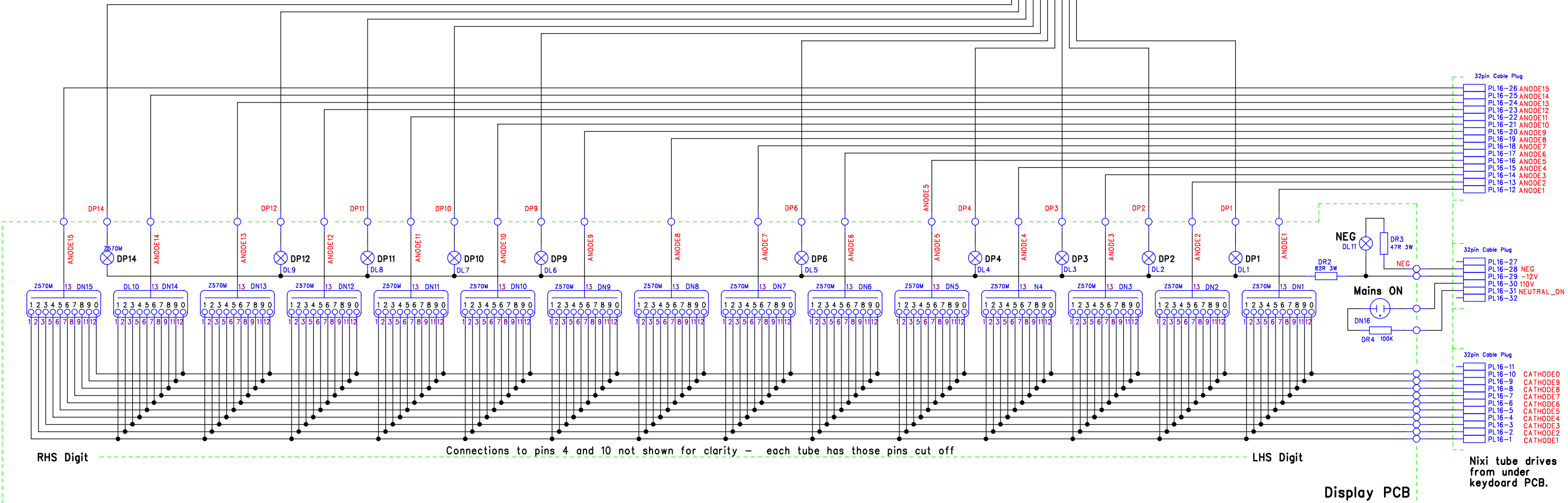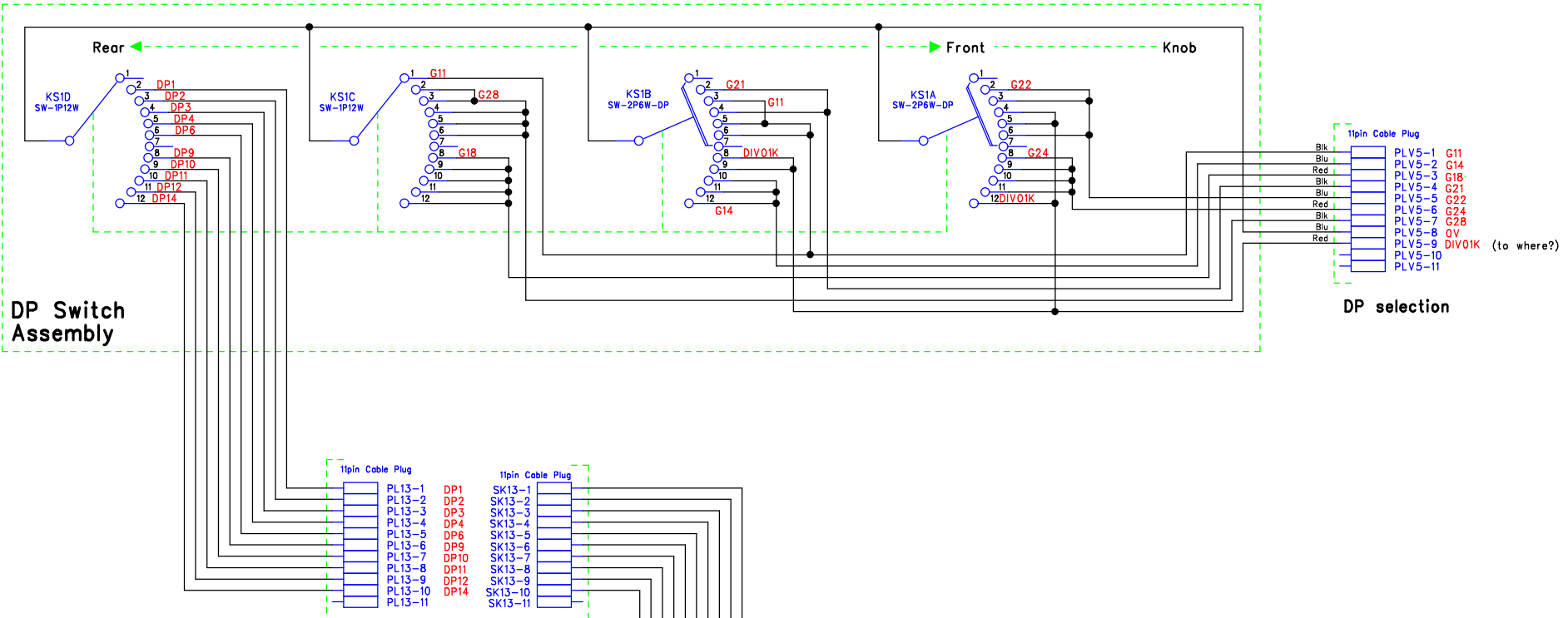

These diagrams are referenced to 0V - Logical 1 = -12v, logical 0 = 0V



© 2017 Mike Hatch. (www.soemtron.org)

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

Pcb Dwg # =

Name	Date
MD Hatch	11/10/2017
Checked	-


Scale	Nts
Sheet	4
Next Sheet	8
Drawing Number	Soemtron 222

Title	Issue	By	Checked
Soemtron ETR 222 Calculator DP Selection and Nixie Display Circuit diagram	A2	Mike Hatch	Mike Hatch


RevNo	Revision note	Date	By	Checked
-	-	-	-	-




RevNo	Revision note	Date	By	Checked
-	-	-	-	-

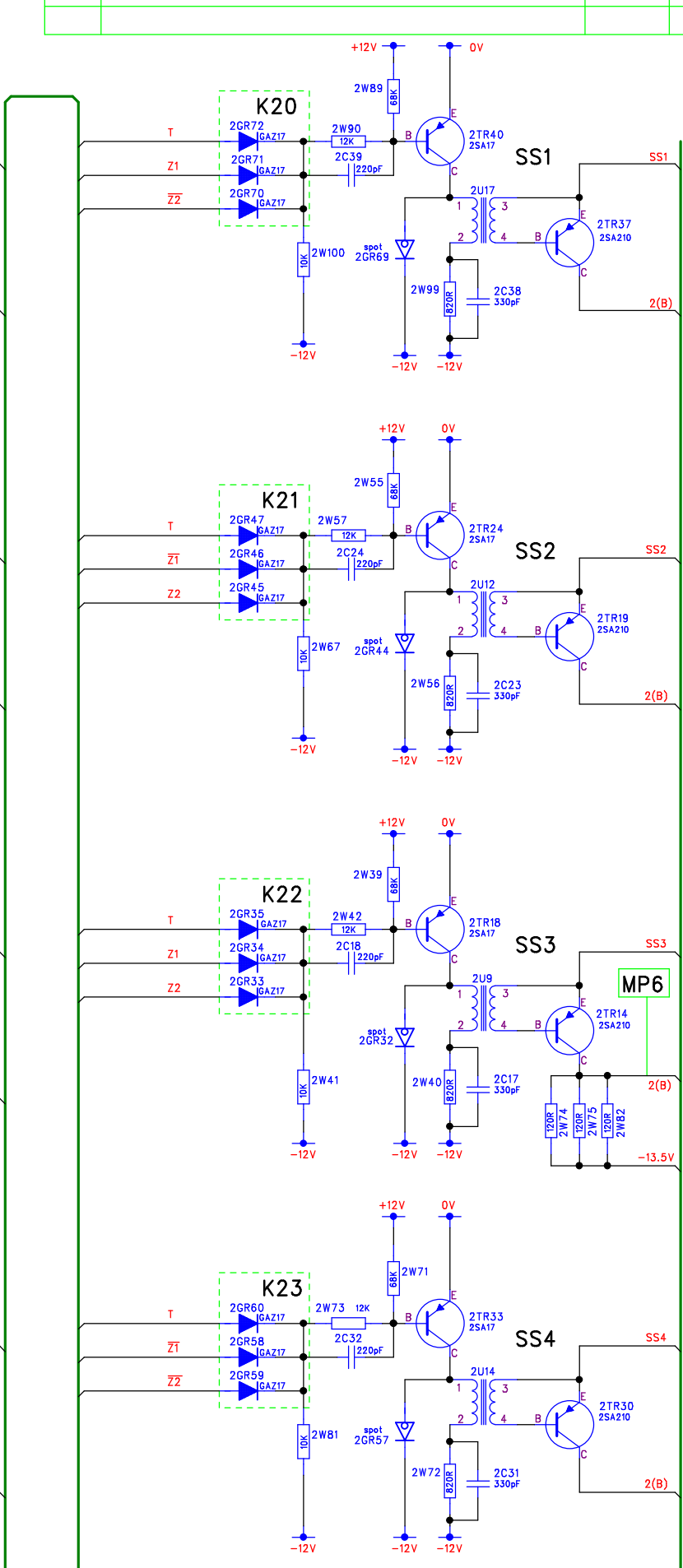

	Name	Date	Sheet	10	Soemtron 222 Calculator Transcribed Misc Circuits Board 2/1 – Core Drivers				
	Drawn	MD Hatch	15/8/2017	Next Sheet					11
	Checked	–	–	Drawing Number					Soemtron 222

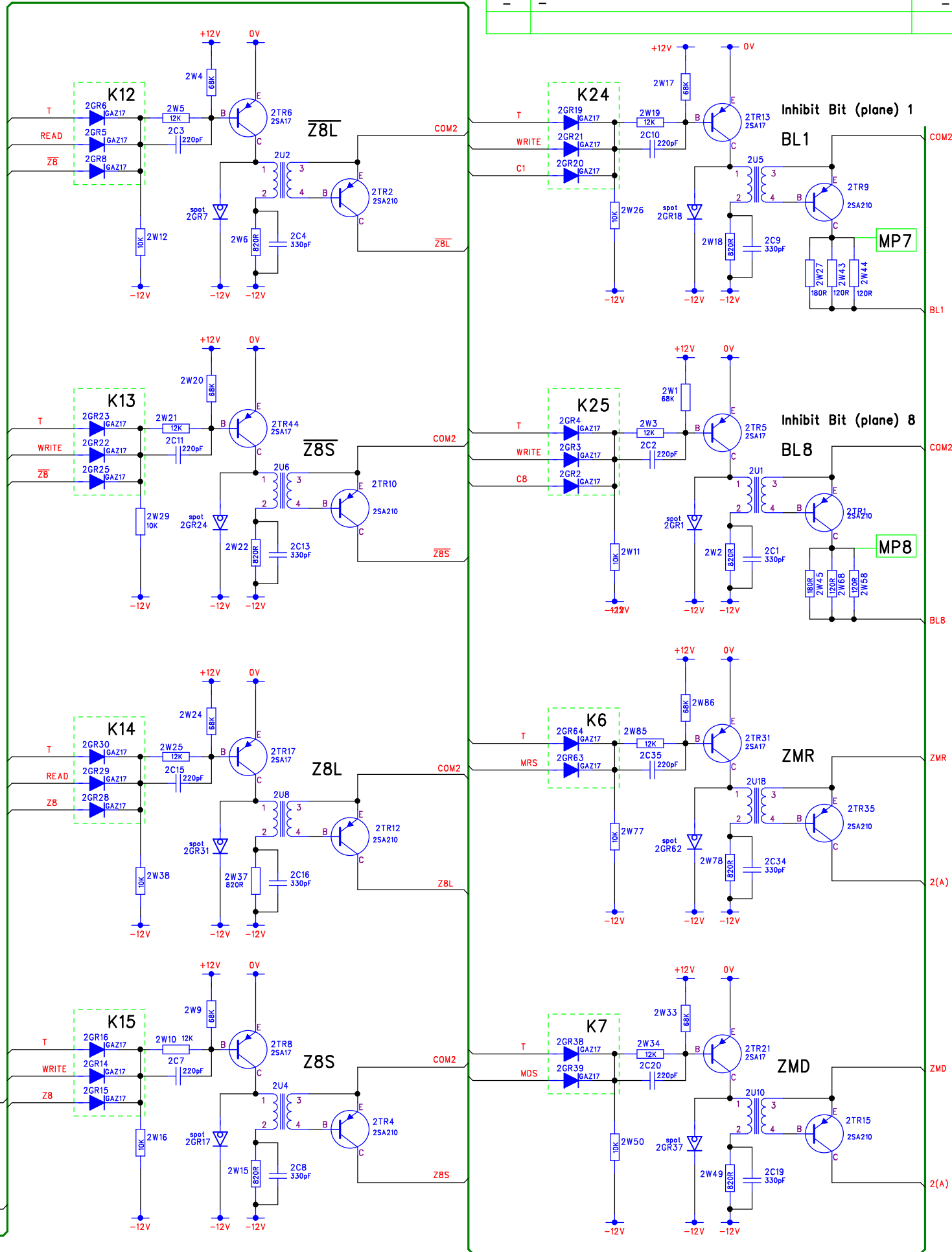

 

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org


	Name	Date	Sheet	12	Soemtron 222 Calculator Transcribed Misc Circuits Board 3/1 – B1, B2, VOR				
	Drawn	MD Hatch	15/8/2017	Next Sheet					13
	Checked	–	–	Drawing Number					Soemtron 222




Pcb Dwg # =

	Name	Date	Sheet	14	Soemtron 222 Transcribed Misc Circuits Board 4/1 – Z Counter, Drive 1,4,17			
	Drawn	MD Hatch	15/8/2017	Next Sheet				
	Checked	–	–	Drawing Number	Soemtron 222	A2	Issue	A



RevNo	Revision note	Date	By	Checked
—	—	—	—	—

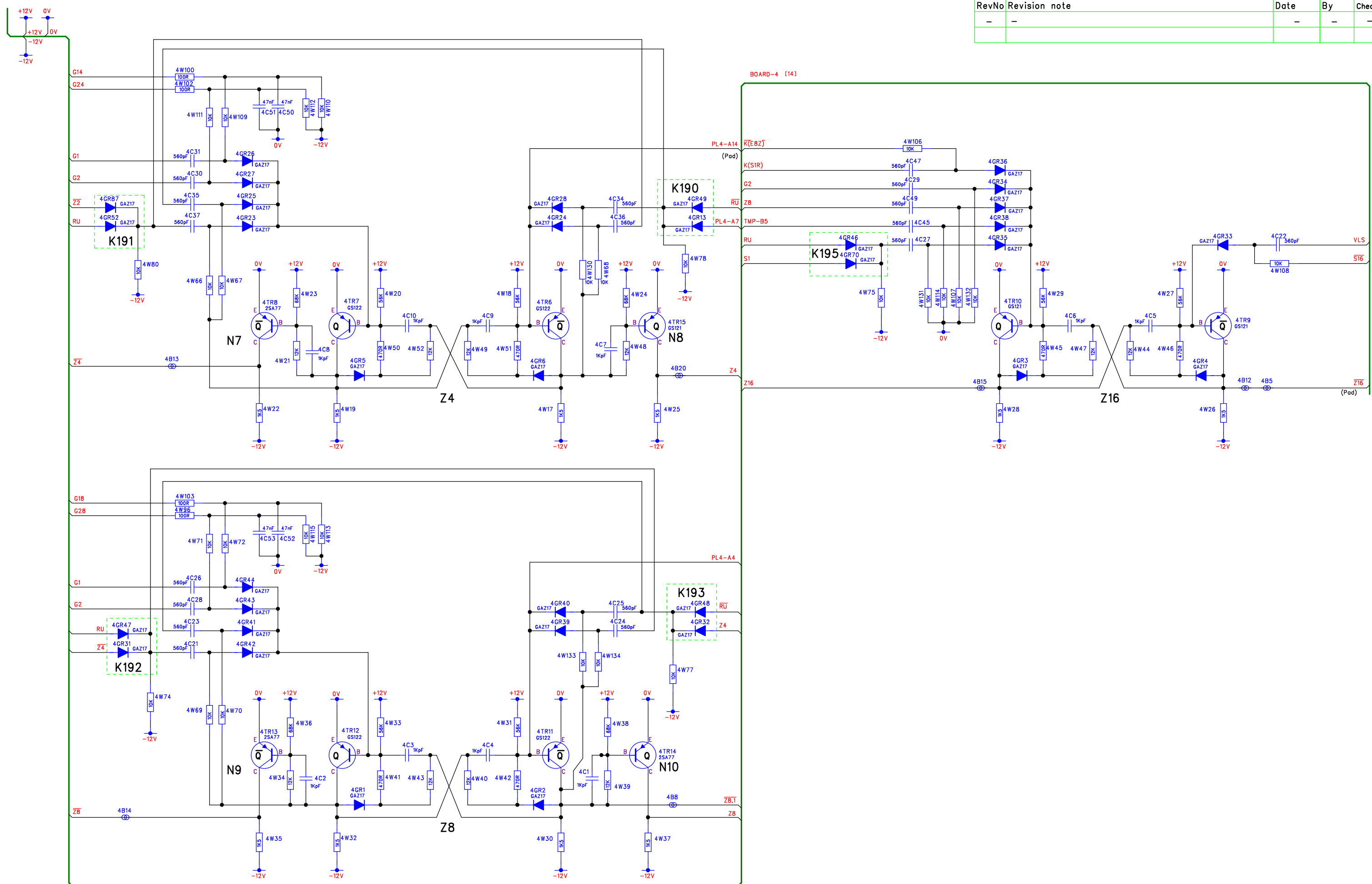

 

Comp side -
Solder side - 3969- 224-307-006-b
Date coded - 35/68

RevNo	Revision note	Date	By	Checked
-	-	-	-	-

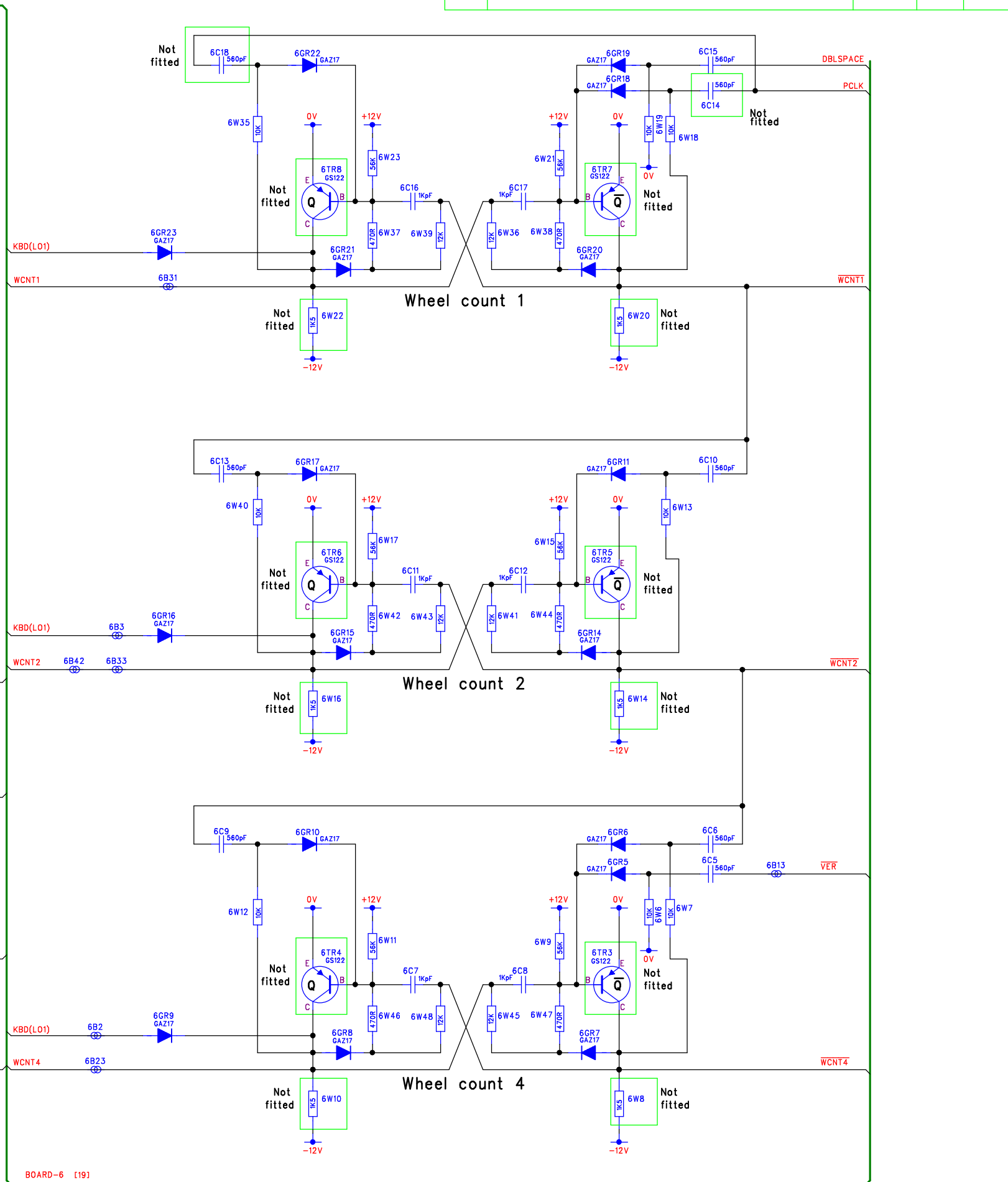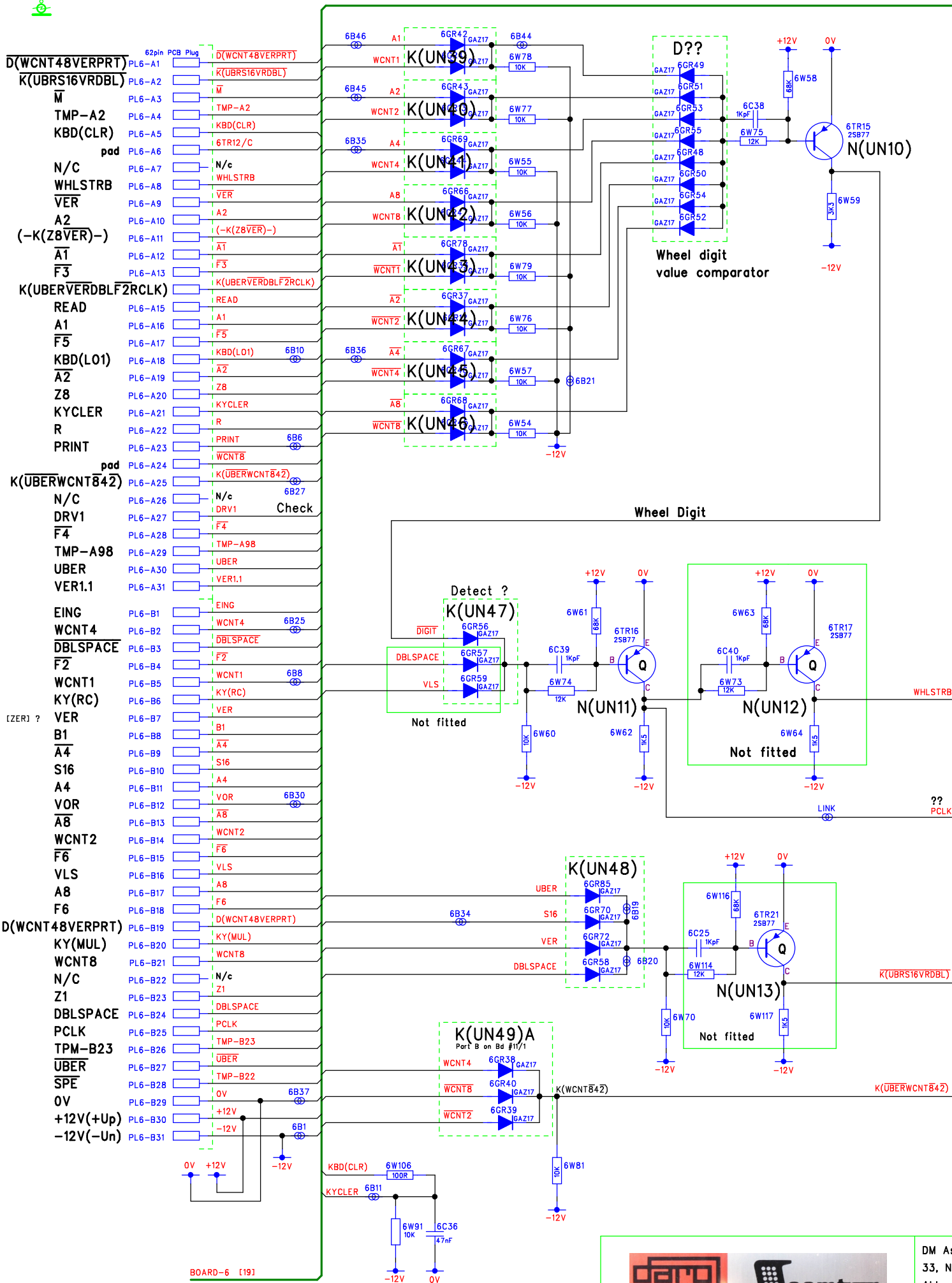


These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V



DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org



Pcb Dwg # =		Scale	Nts	Title	
Drawn	Name	Date	Sheet	Soemtron ETR 222 Calculator	
Checked	MD Hatch	15/8/2017	Next Sheet	Transcribed Misc Circuits	
			Drawing Number	Board 6/1 - Wheel Count (1, 2, 4)	
				Soemtron 222	
				A2 Issue A	

 

© 2017 Mike Hatch. (www.soemtron.org)

	Name	Date	Sheet	20	Soemtron 222 Calculator			
Drawn	MD Hatch	15/8/2017	Next Sheet	21	Transcribed Misc Circuits			
Checked	—	—	Drawing Number	Soemtron 222	A2	Issue	A	

RevNo	Revision note	Date	By	Checked
–	–	–	–	–

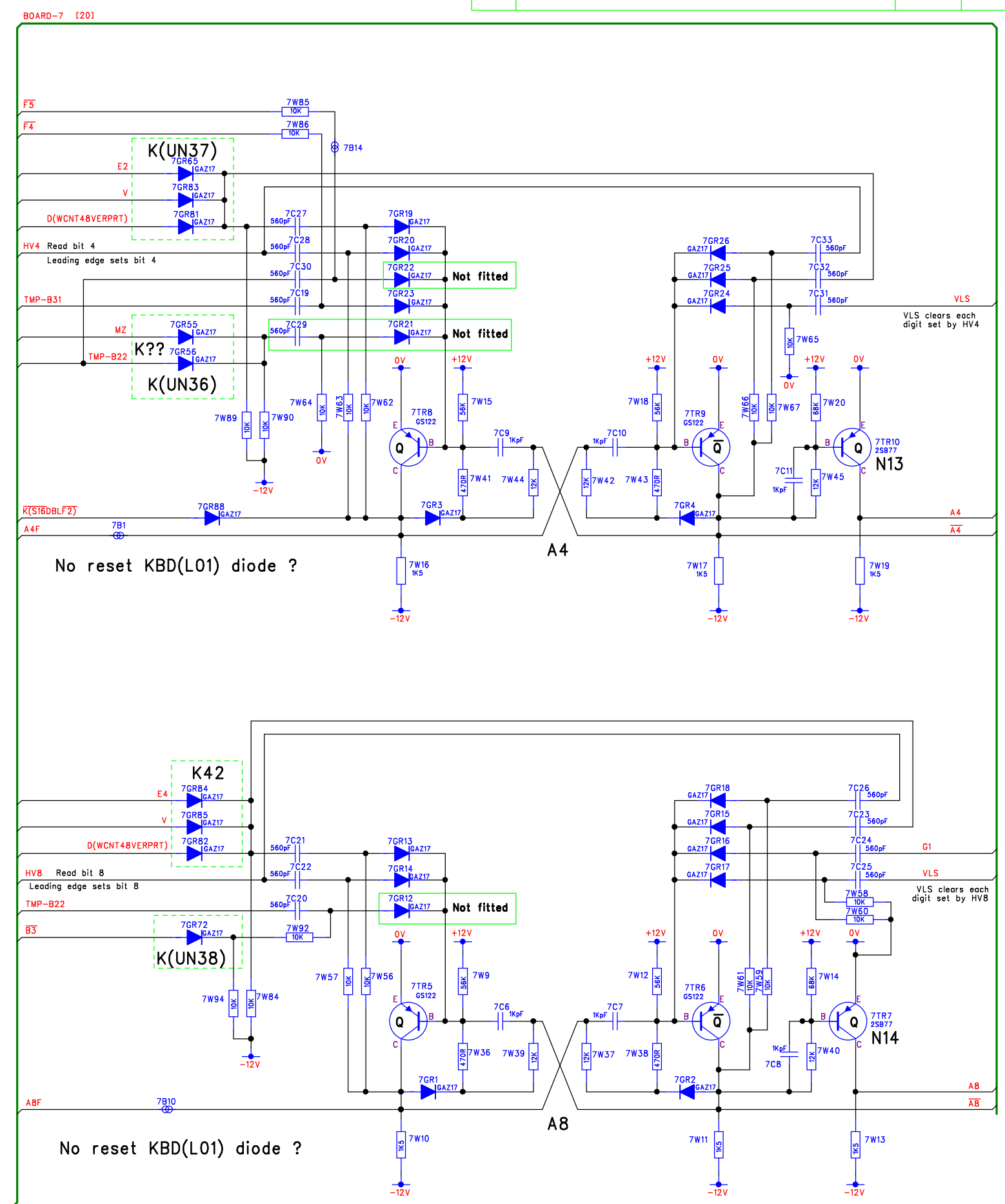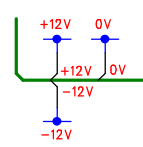

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

Pcb Dwg # =

	Name	Date
Drawn	MD Hatch	15/8/2017
Checked	—	—


Scale	Nts
Sheet	21
xt Sheet	22
Drawing Number	

Title Soemtron ETR 222 Calculator Transcribed Misc Circuits Board 7/2 - A Register (A4, A8)			
Soemtron 222	A2	Issue	A

These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V

Comp side -
Solder side - 3952- 224-307-008-a
Date coded - 40/69

RevNo	Revision note	Date	By	Checked
-	-	-	-	-

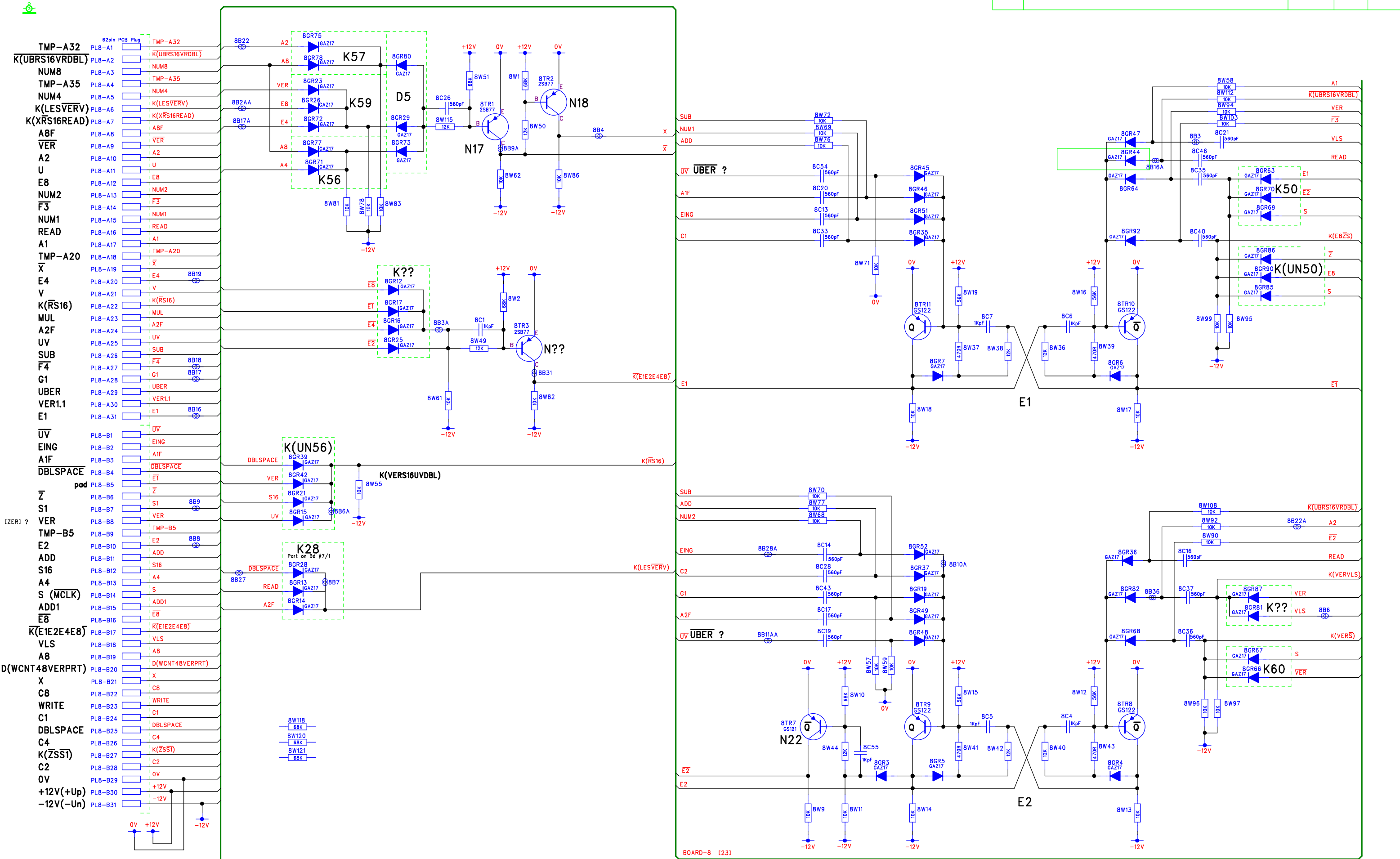

These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V




© 2017 Mike Hatch. (www.soemtron.org)

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

Pcb Dwg # =			Scale	Nts	Title		
			Sheet	22	Soemtron ETR 222 Calculator		
Drawn			Next Sheet	23	Transcribed Misc Circuits		
Checked			Drawing Number		Board 8/1 - E Register (E1, E2)		
					Soemtron 222		
					A2 Issue A		

RevNo	Revision note	Date	By	Checked
—	—	—	—	—

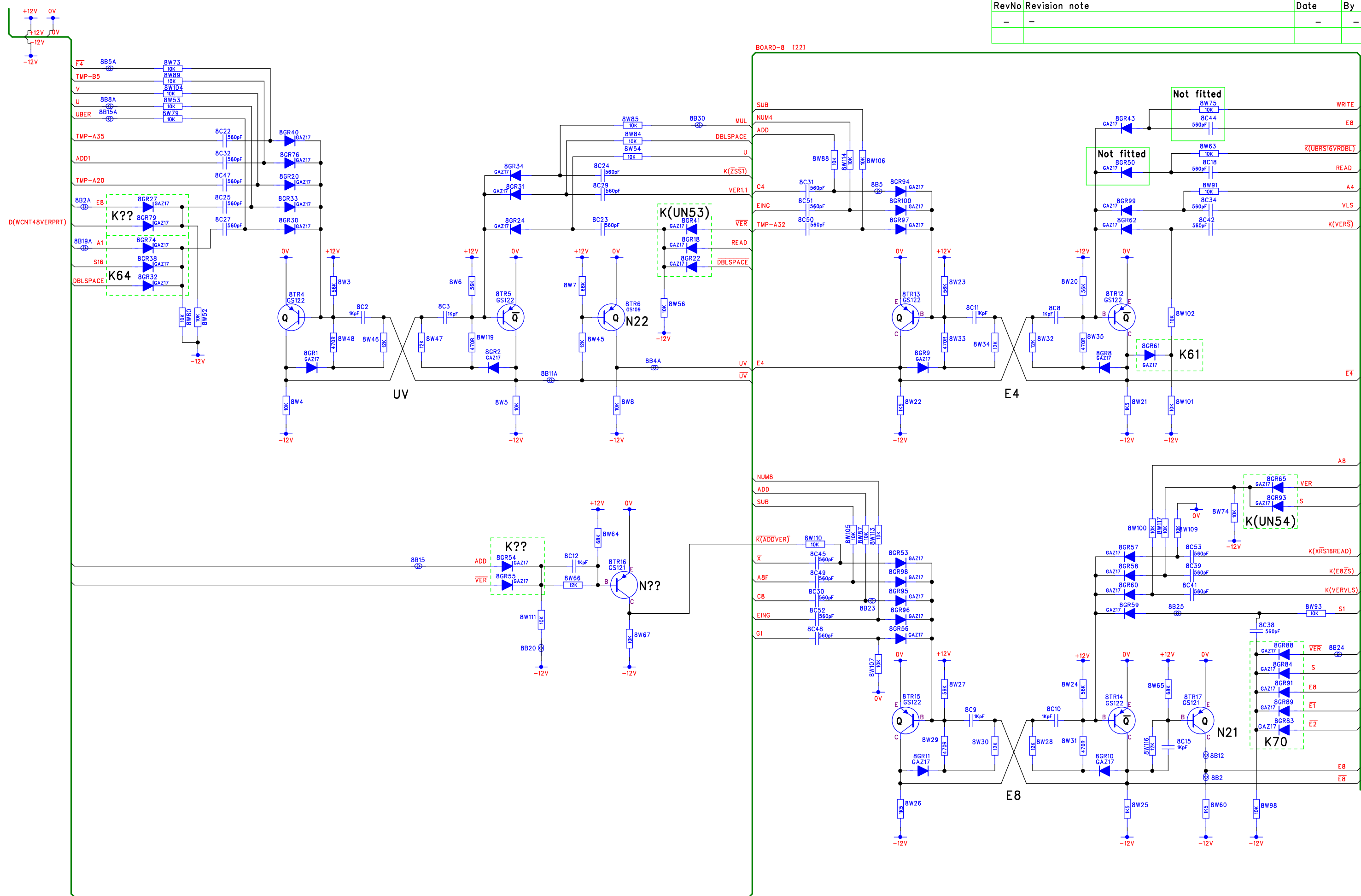

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

Pcb Dwg # =

	Name	Date	Sheet	23	Soemtron 222 - E4, E8 Transcribed Misc Circuits Board 8/2 – E Register (E4, E8)			
	Drawn	MD Hatch	15/8/2017	Next Sheet				
	Checked	–	–	Drawing Number	Soemtron 222	A2	Issue	A


These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V



© 2018 Mike Hatch. (www.soemtron.org)


Pcb Dwg # =

	Name	Date	Sheet	24	Soemtron 222 Calculator Transcribed Misc Circuits Board 9 /1 – Read/Write, S1, V			
	Drawn	MD Hatch	1/2/2018	Next Sheet				25
	Checked	–	–	Drawing Number				Soemtron 222

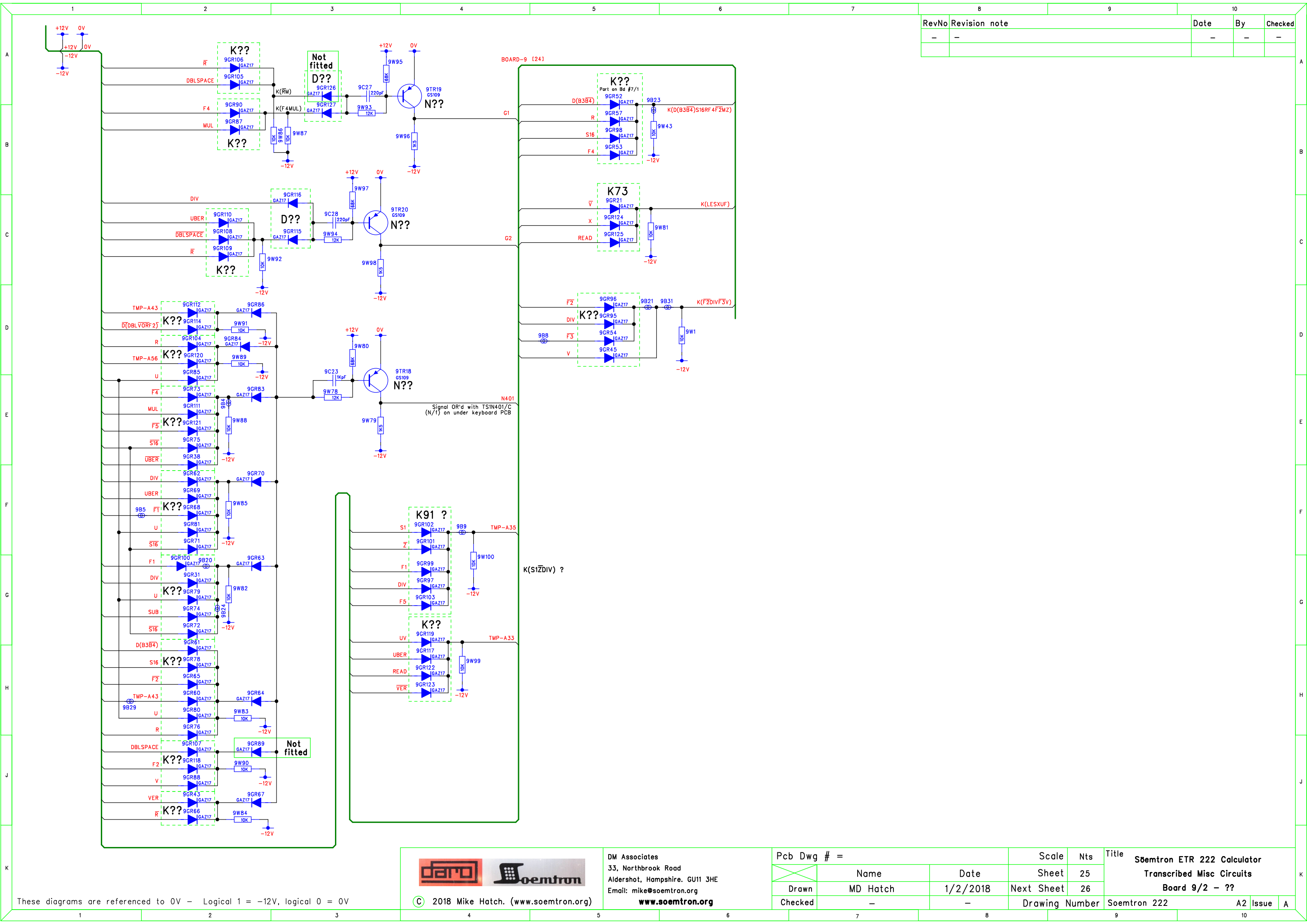

Comp side -
Solder side - 224-307-010a 3970
Date coded - 34/68

RevNo	Revision note	Date	By	Checked
-	-	-	-	-

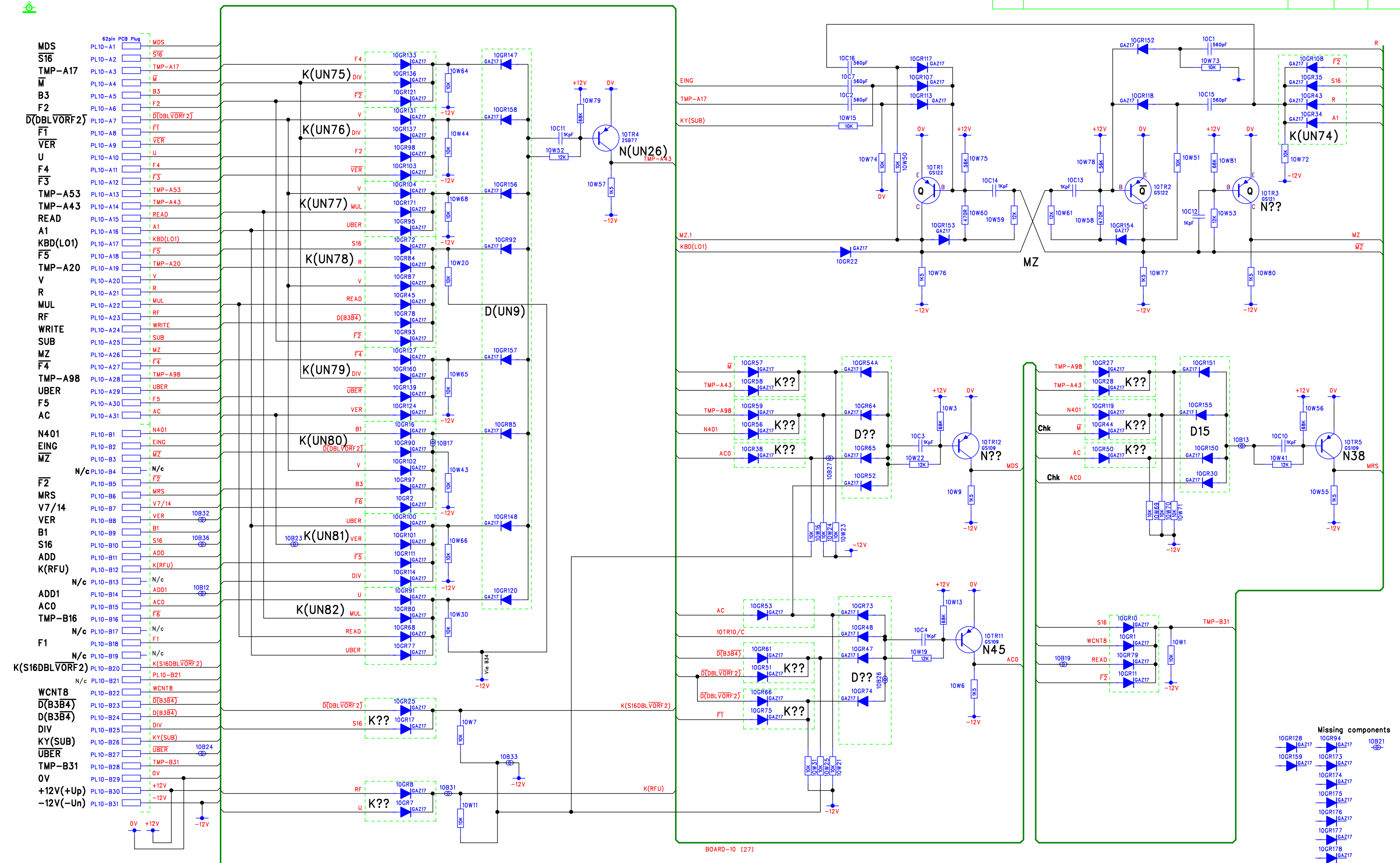

These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V



© 2018 Mike Hatch. (www.soemtron.org)

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

Pcb Dwg # =

Name	Date
MD Hatch	15/8/2017
Checked	-

Scale

Nts


Title

Soemtron ETR 222 Calculator
Transcribed Misc Circuits
Board 10/1 - 3MZ + Gating


Sheet 26
Next Sheet 27
Drawing Number

Soemtron 222

A2 Issue A

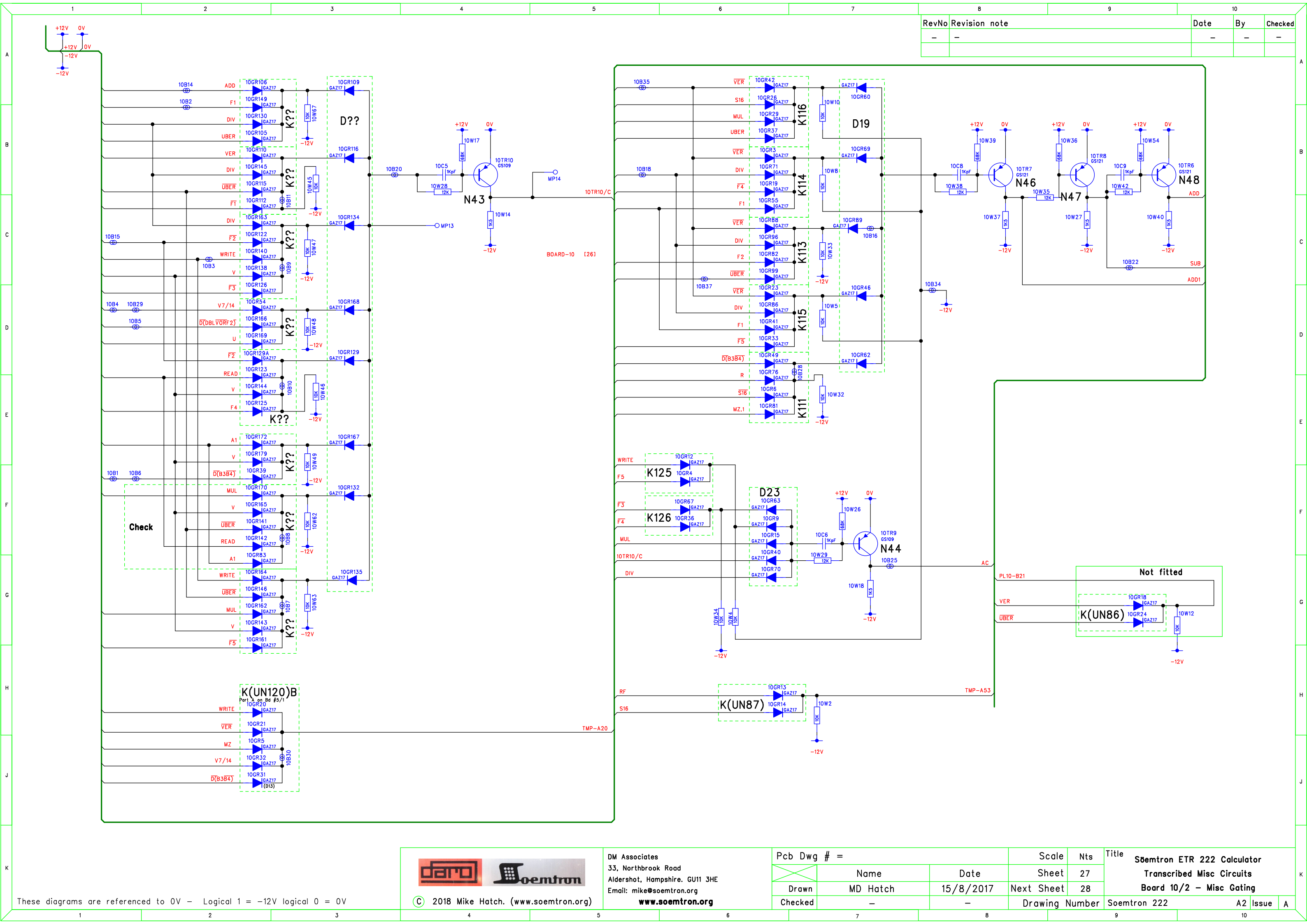


RevNo	Revision note	Date	By	Checked
-	-	-	-	-

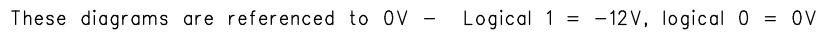

© 2018 Mike Hatch. (www.soemtron.org)

	Name	Date	Sheet	28	Transcribed Misc Circuits Board 11/1 – UBER & ?			
	Drawn	MD Hatch	8/10/2018	Next Sheet				
	Checked	–	–	Drawing Number	Soemtron 222	A2	Issue	A

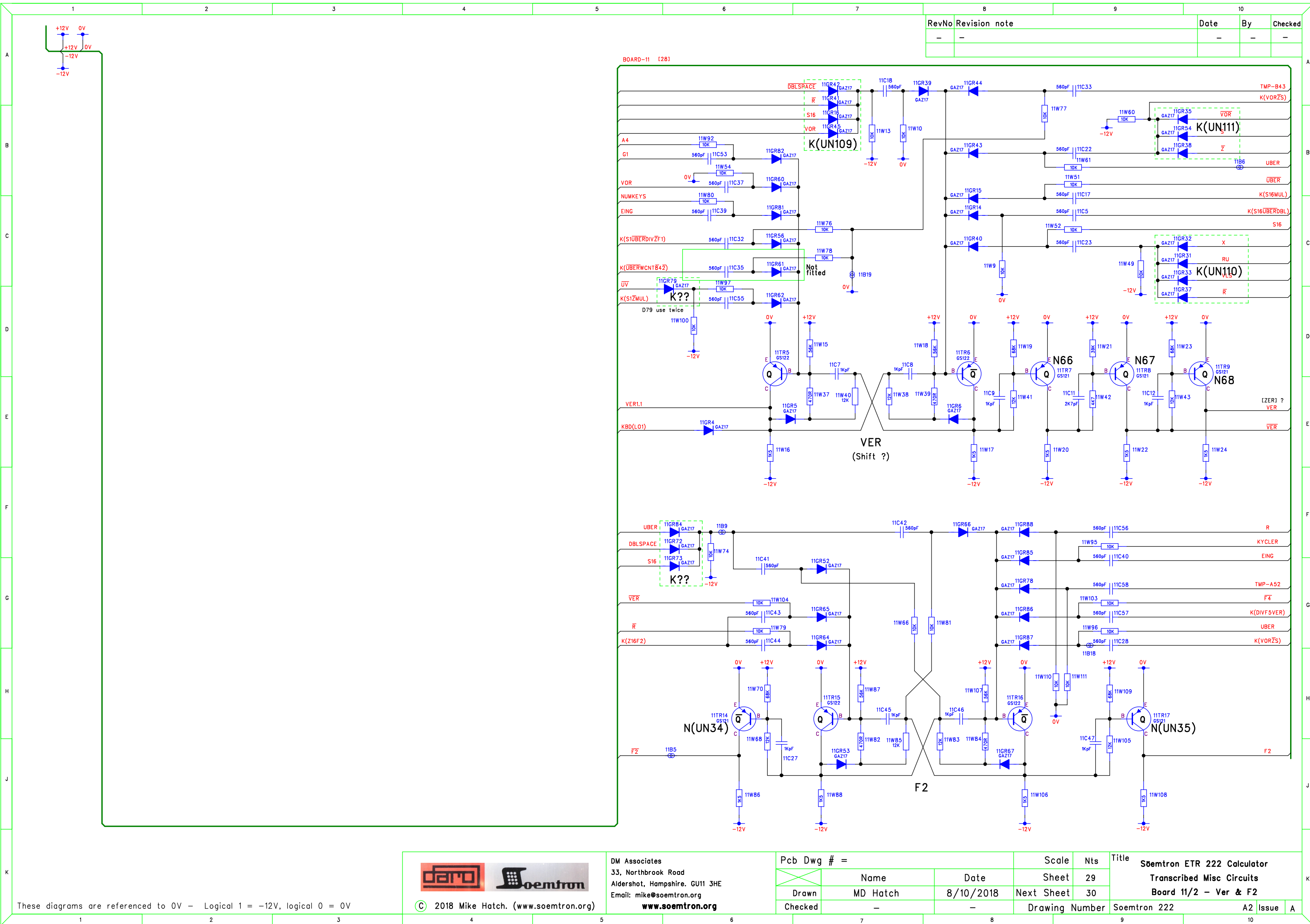Title Soemtron ETR 222 Calculator
 Transcribed Misc Circuits
 Board 11/1 – UBER & ?






DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

	Name	Date	Sheet	30	Soemtron 222 Calculator Transcribed Misc Circuits Board 12/1 – F1 & F5				
	Drawn	MD Hatch	15/10/2018	Next Sheet					31
	Checked	–	–	Drawing Number					Soemtron 222

RevNo	Revision note	Date	By	Checked
–	–	–	–	–

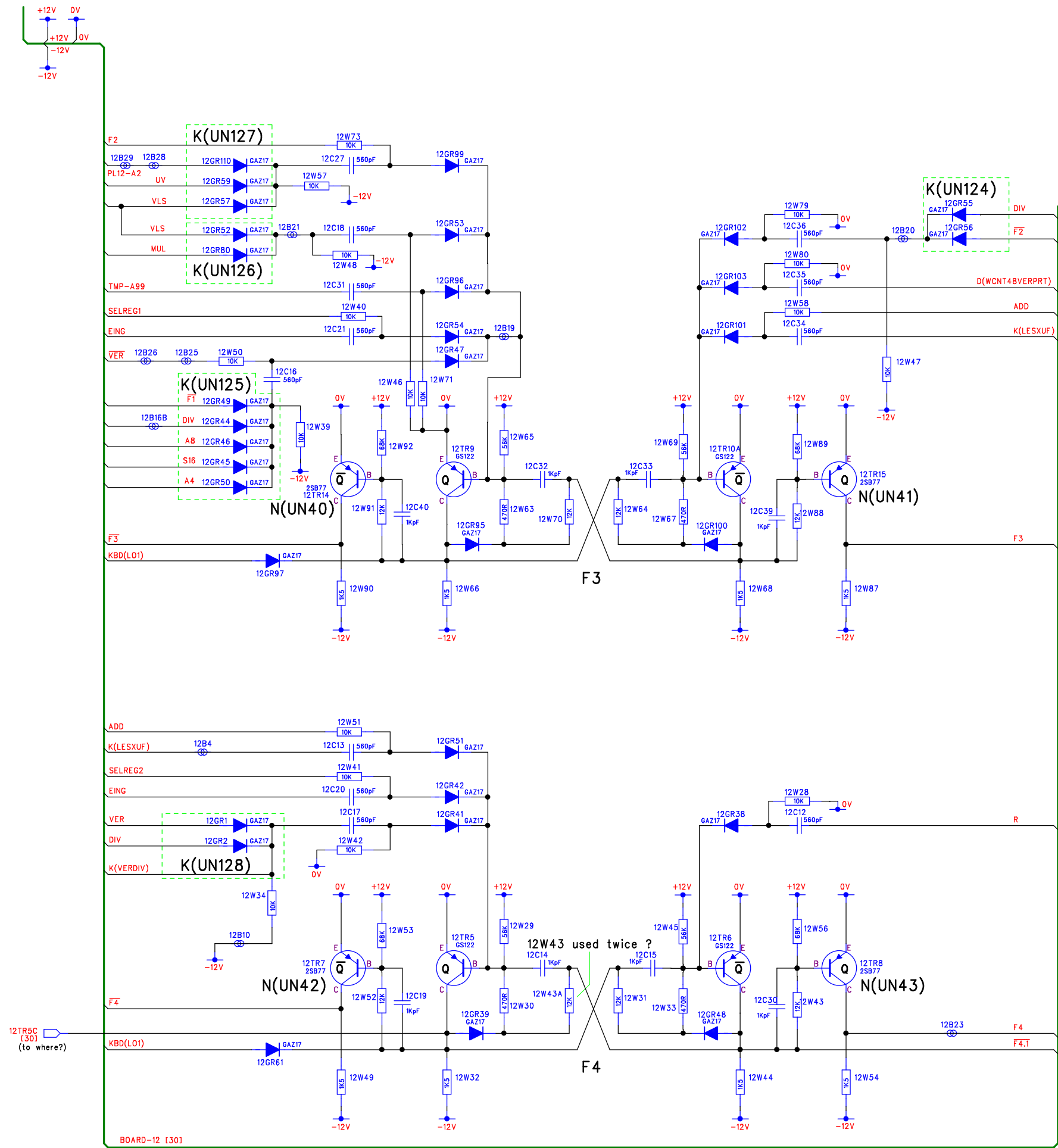


Pcb Dwg # =			Scale	Nts	Title Soemtron ETR 222 Calculator Transcribed Misc Circuits Board 12/2 – F3 & F4		
	Name	Date	Sheet	31			
Drawn	MD Hatch	15/10/2018	Next Sheet	32			
Checked	—	—	Drawing Number				
			Soemtron 222		A2	Issue	A


These diagrams are referenced to 0V - Logical 1 = -12V, logical 0 = 0V

DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

RevNo	Revision note	Date	By	Checked
-	-	-	-	-

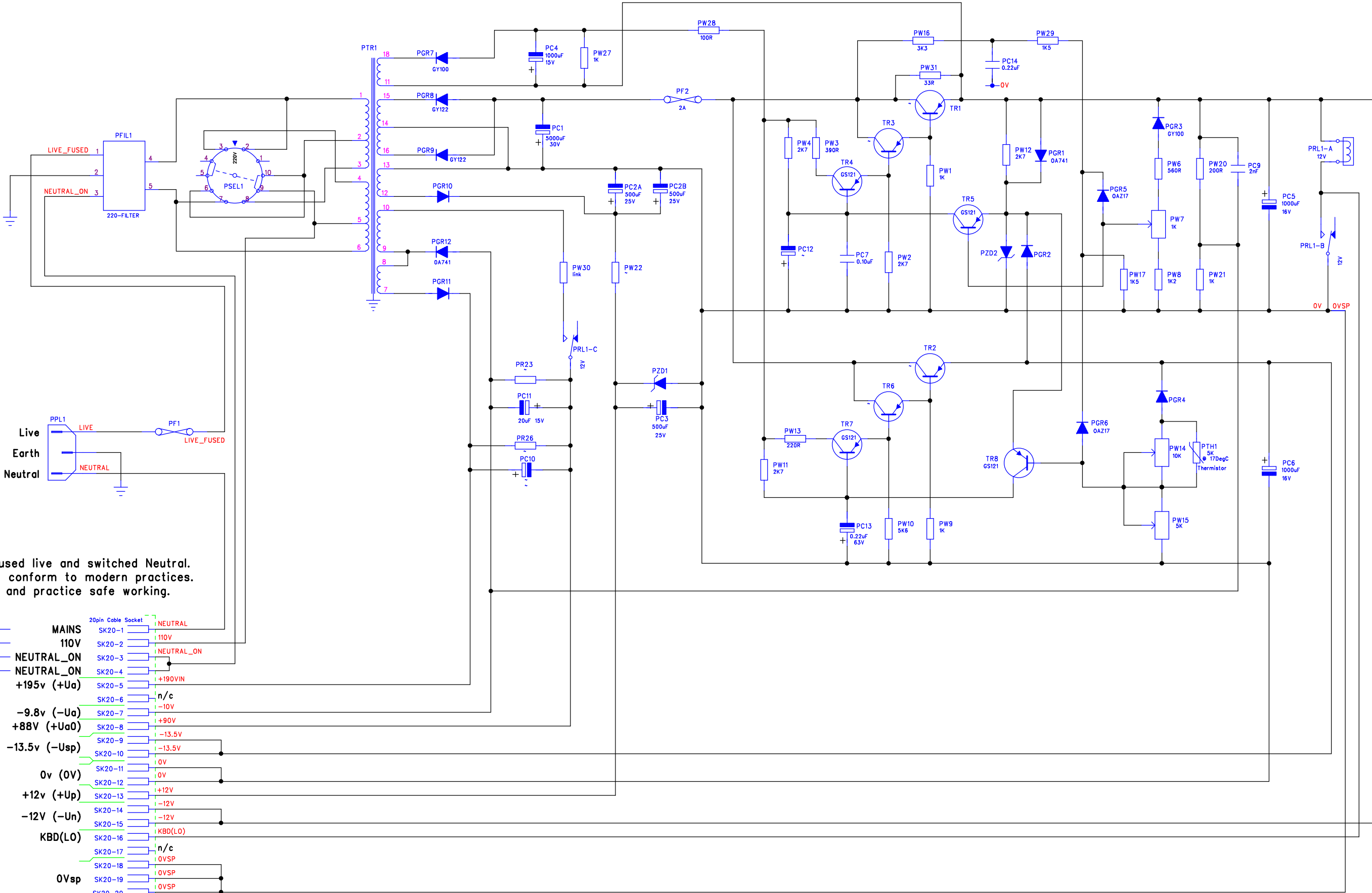

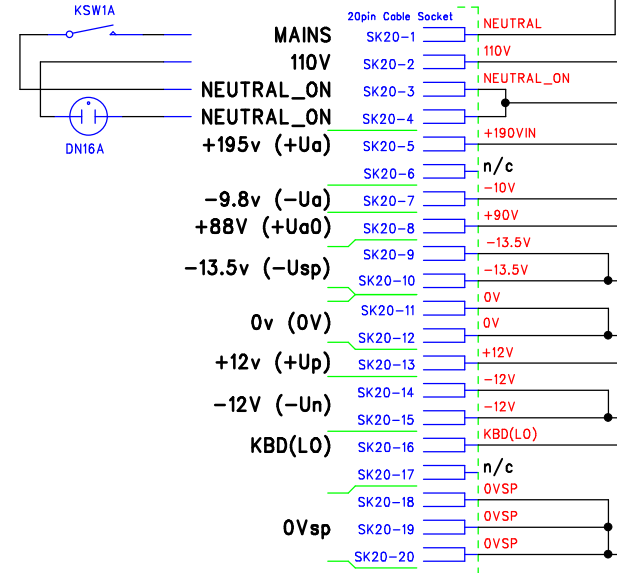The 222 is Fused live and switched Neutral.
This does not conform to modern practices.
Exercise care and practice safe working.



DM Associates
33, Northbrook Road
Aldershot, Hampshire. GU11 3HE
Email: mike@soemtron.org
www.soemtron.org

© 2017 Mike Hatch. (www.soemtron.org)

Pcb Dwg # =

Name	Date
MD Hatch	30/1/2024
Checked	-

Scale

Nts

Sheet	32
Next Sheet	33
Drawing Number	Soemtron 222

Title

Soemtron ETR 222 Calculator
Power Supply Wiring
Circuit Diagram

